

- Gate networks
- Sets of gates: (AND OR NOT), NAND NOR XOR
- Analysis and description of gate networks

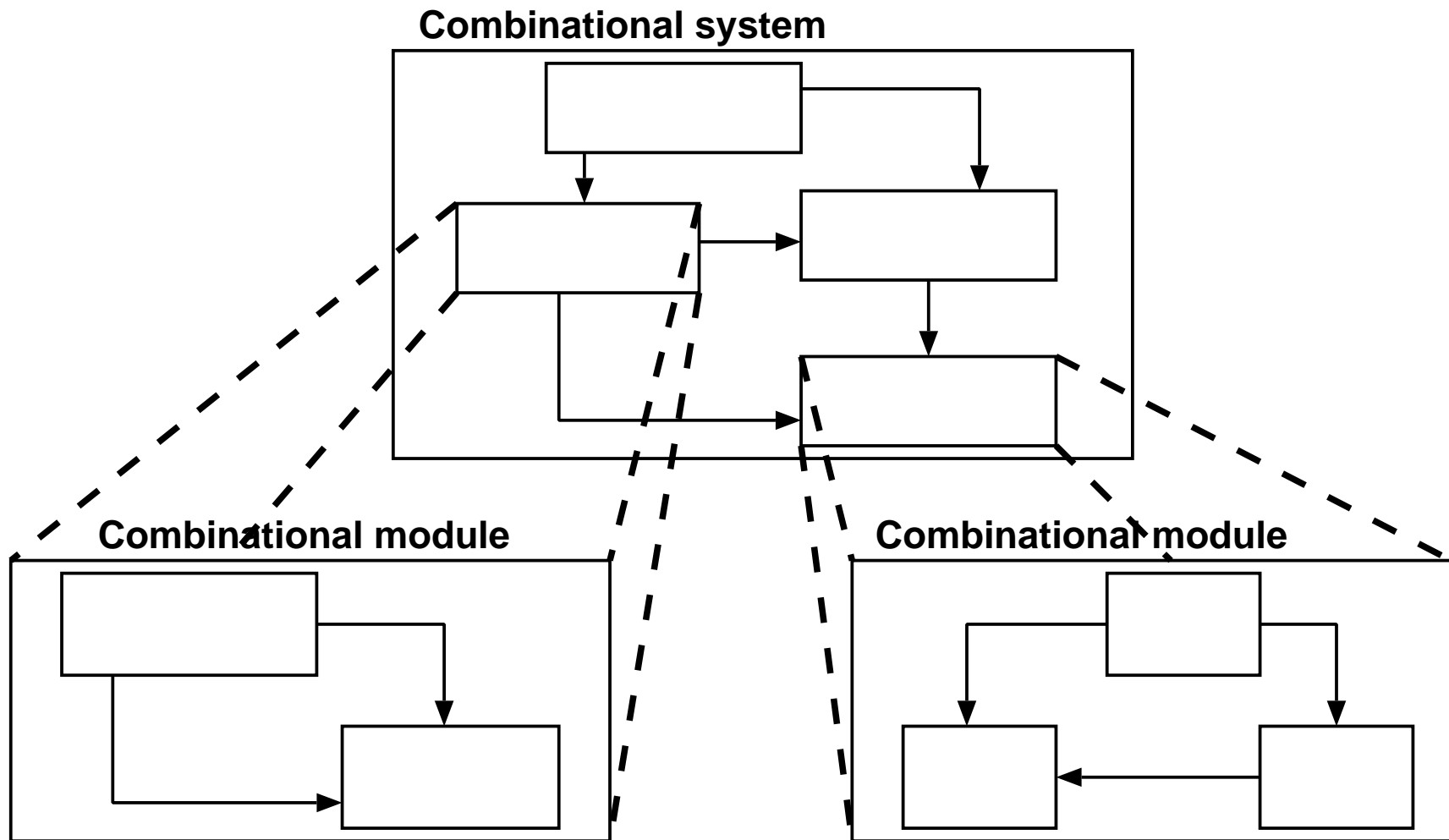


Figure 4.1: Hierarchical implementation of a module

 


Figure 4.2: A gate network

- gates
- external inputs and outputs
- connections

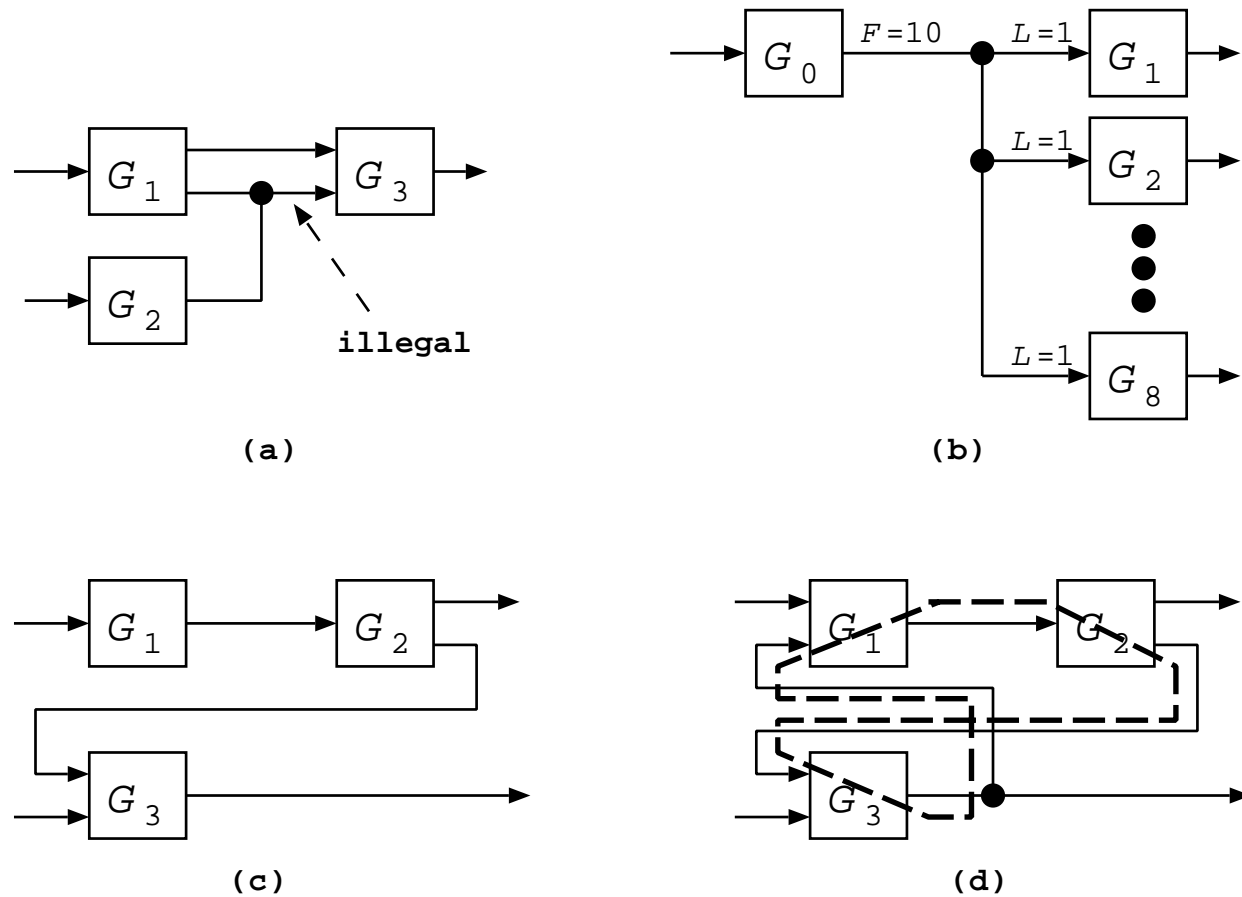


Figure 4.3: a) Illegal network connection. b) Acceptable output load. c) Loop-free network. d) Loop network

- logic diagram (graphical representation)
- net list (tabular representation)
- HDL description (program)

 


Figure 4.4: a) Graphical representation (logic diagram)

Gate	Type	Inputs	Output
A	AND – 2	$A_1$	$A_3$
B	AND – 3	$A_2$ $B_1$ $B_2$ $B_3$	$B_4$
C	OR – 2	$C_1$ $C_2$	$C_3$

Gates

From	To
$x_3$	$A_1$
$x_2$	$A_2$
$x_2$	$B_1$
$x_1$	$B_2$
$x_0$	$B_3$
$A_3$	$C_1$
$B_4$	$C_2$
$C_3$	$z$

Connections

(b)

```

A_3 <= x3 and x2;
B_4 <= x2 and x1 and x0;
C_3 <= A_3 or B_4;
z    <= C_3;

```

(c)

Figure 4.4: Network representation: a) graphical; b) tabular; c) HDL-based.

- functional specification
- input load factors of the network inputs;
- fan-out factor of the network outputs (only for some technologies); and
- propagation delays through the network.

- Set {AND, OR, NOT}

$$z = (((x_0 + x_1)x_2)' + x_2x_3 + x_4)'$$

 


Figure 4.5: Correspondence among switching expression and AND-OR-NOT network



## Universal sets of gates (cont.)

- Sets  $\{\text{AND}, \text{NOT}\}$  and  $\{\text{OR}, \text{NOT}\}$

$$x_{n-1} + x_{n-2} + \dots + x_i + \dots + x_0 = (x'_{n-1} x'_{n-2} \dots x'_i \dots x'_0)'$$

 


Figure 4.6: AND-NOT implementation of an OR gate

## Universal sets of gates (cont.)

---

- Sets {NAND} and {NOR}

$$x' = (xx)'$$

$$NOT(x) = NAND(x, x)$$

$$x_1x_0 = ((x_1x_0)')' = ((x_1x_0)'(x_1x_0)')'$$

$$AND(x_1, x_0) = NAND(NAND(x_1, x_0), NAND(x_1, x_0))$$

## Universal sets of gates (cont.)

---

 


Figure 4.7: Implementations with NAND gates: a) NOT; b) AND

 


Figure 4.8: Mixed-logic notation: a) NAND gate b) NOR gate

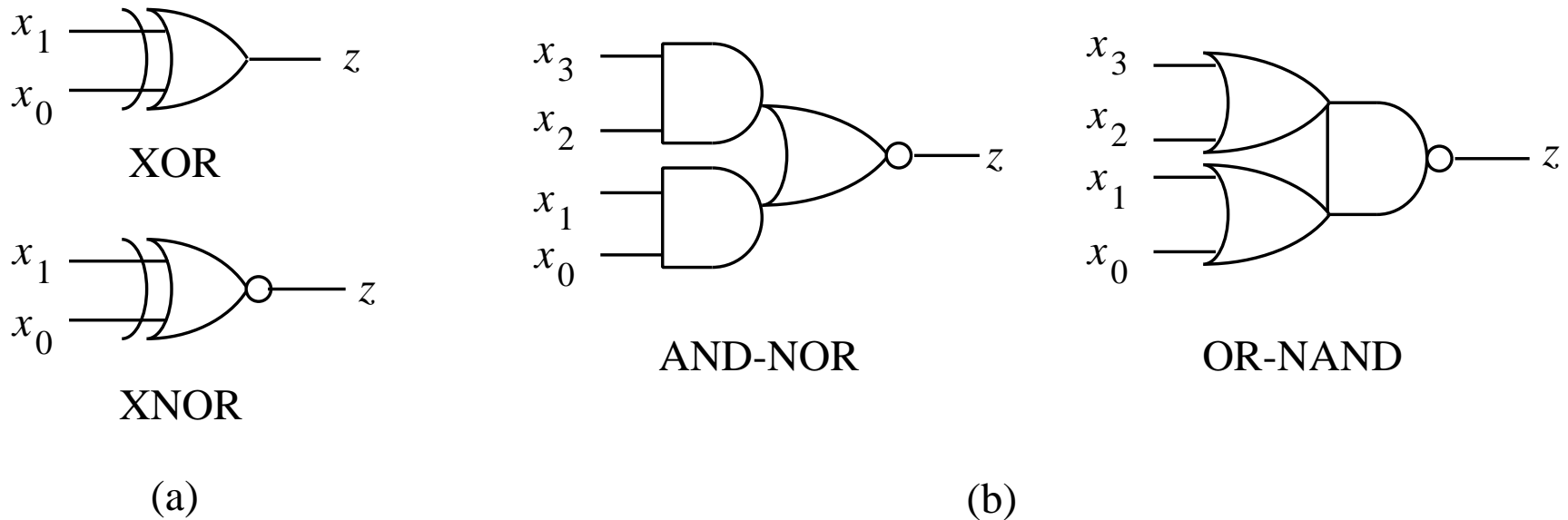


Figure 4.9: Additional gates in CMOS a) XOR and XNOR, b) Complex gate structures: AND-OR and OR-AND

- Functional analysis:
  1. Obtain I/O switching expressions
  2. Obtain a tabular representation of the (binary) function
  3. Define high-level input and output variables;  
    use codes to relate these variables with the bit-vectors
  4. Obtain a high-level specification of the system
  
- Network characteristics:  
    input load factors, fan-out factors, and delays

## Obtain switching expressions

---

- i) Assign names to each connection in the network
- ii) Write switching expressions for each gate output
- iii) Substitute all internal names to obtain external outputs in terms of external inputs.

 


Figure 4.10: Gate network for analysis



Output expressions:

$$\begin{aligned} z_0 &= T_2 + T_3 \\ &= x'_0 x'_1 x_2 + x_0 T_1 \\ &= x'_0 x'_1 x_2 + x_0 (x'_2 + x_3) \\ &= x'_0 x'_1 x_2 + x_0 x'_2 + x_0 x_3 \end{aligned}$$

$$\begin{aligned} z_1 &= T_5 + T_6 \\ &= x_1 x_2 x_3 + T'_4 \\ &= x_1 x_2 x_3 + (T_1 x'_0 x_1)' \\ &= x_1 x_2 x_3 + T'_1 + x_0 + x'_1 \\ &= x_1 x_2 x_3 + x_2 x'_3 + x_0 + x'_1 \end{aligned}$$

Reduced expressions

$$\begin{aligned} z_0 &= x'_0 x'_1 x_2 + x_0 x'_2 + x_0 x_3 \quad (\text{no reduction possible}) \\ z_1 &= x_0 + x'_1 + x_2 \end{aligned}$$

## Hierarchical approach

---

- decompose the network into subnetworks (modules)
- analyze each subnetwork separately
- use substitution to obtain the network function

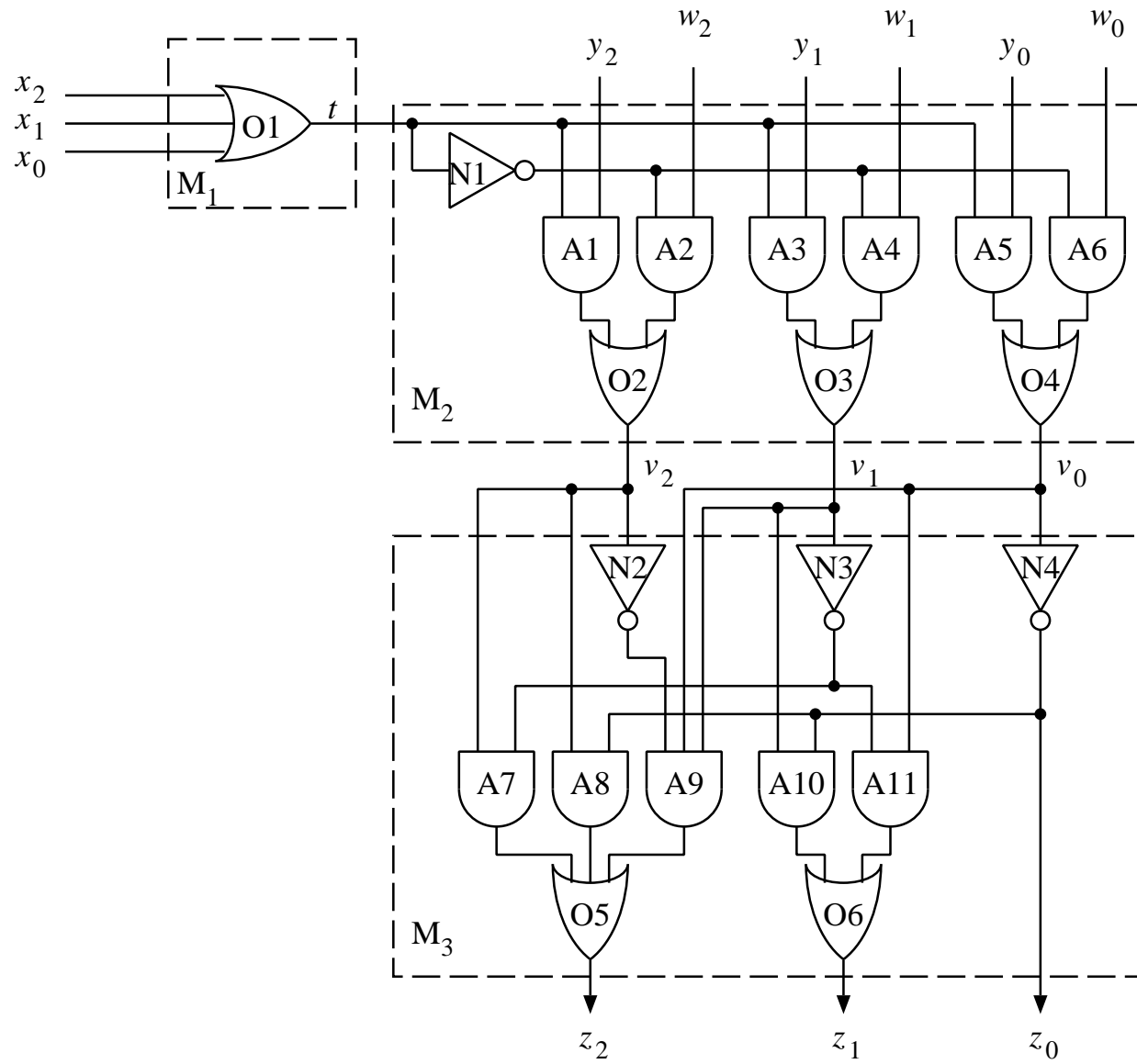


Figure 4.11: Network for hierarchical analysis

## Example cont.

---

Verify that the network satisfies specification:

Inputs:  $x, y, w \in \{0, 1, \dots, 7\}$

Output:  $z \in \{0, 1, \dots, 7\}$

Function:  $z = \begin{cases} (y + 1) \bmod 8 & \text{if } x \neq 0 \\ (w + 1) \bmod 8 & \text{if } x = 0 \end{cases}$

- Subnetworks

$M_1$ :

$$t = x_2 \mathbf{+} x_1 \mathbf{+} x_0$$

$$t = \begin{cases} 1 & \mathbf{if} \ x \neq 0 \\ 0 & \mathbf{otherwise} \end{cases}$$

$M_2$ :

$$v_i = y_i t \mathbf{+} w_i t' \quad (i = 0, 1, 2)$$

$$\underline{v} = \begin{cases} \underline{y} & \mathbf{if} \ t = 1 \\ \underline{w} & \mathbf{if} \ t = 0 \end{cases}$$

$$v = \begin{cases} y & \mathbf{if} \ t = 1 \\ w & \mathbf{if} \ t = 0 \end{cases}$$

$M_3$ :

$$z_2 = v'_2 v_1 v_0 \mathbf{+} v_2 v'_1 \mathbf{+} v_2 v'_0$$

$$z_1 = v_1 v'_0 \mathbf{+} v'_1 v_0$$

$$z_0 = v'_0$$

## Example (cont.)

---

- High-level specification:

$v_2$	$v_1$	$v_0$	$z_2$	$z_1$	$z_0$		$v$	$z$
0	0	0	0	0	1		0	1
0	0	1	0	1	0		1	2
0	1	0	0	1	1		2	3
0	1	1	1	0	0	→	3	4
1	0	0	1	0	1		4	5
1	0	1	1	1	0		5	6
1	1	0	1	1	1		6	7
1	1	1	0	0	0		7	0

From table, we get

$$z = (v + 1) \bmod 8$$

Second level of analysis:

$$z = \begin{cases} (y + 1) \bmod 8 & \mathbf{if} \ x \neq 0 \\ (w + 1) \bmod 8 & \mathbf{if} \ x = 0 \end{cases}$$

# Analysis of networks with NOT, NAND and NOR

 


Figure 4.12: a) NAND network; b) Network redrawn in mixed-logic notation

- 
- Use mixed-logic transformations

$$\begin{aligned} z &= x'_5 + (x_4 + x'_3)(x'_2 + x_1x'_0) \\ &= x'_5 + x_4x'_2 + x_3x'_2 + x_4x_1x'_0 + x'_3x_1x'_0 \end{aligned}$$



 
 
 


Figure 4.13: a) NOR network; b) Network redrawn in mixed-logic notation

---

$$\begin{aligned} z &= ((x_2 + x'_1)(x'_2 + x_1) + x_0)(x'_2 + x'_1 + x'_0) \\ &= (x_2 + x'_1 + x_0)(x'_2 + x_1 + x_0)(x'_2 + x'_1 + x'_0) \\ &= (x_2x_1 + x'_2x'_1 + x_0)(x'_2 + x'_1 + x_0) \\ &= x'_2x'_1 + x_0 \end{aligned}$$

## Analysis of Characteristics

---

- Load factor of a network input
- Fan-out factor of a network output
- Size of the network
- Network (propagation) delay
- Number of levels of a network
- Dynamic characteristics

Table 4.3: Characteristics of a family of CMOS gates

Gate type	Fan-in	Propagation delays		Load factor	Size [equiv. gates]
		$t_{pLH}$ [ns]	$t_{pHL}$ [ns]	[standard loads]	
AND	2	$0.15 + 0.037L$	$0.16 + 0.017L$	1.0	2
AND	3	$0.20 + 0.038L$	$0.18 + 0.018L$	1.0	2
AND	4	$0.28 + 0.039L$	$0.21 + 0.019L$	1.0	3
OR	2	$0.12 + 0.037L$	$0.20 + 0.019L$	1.0	2
OR	3	$0.12 + 0.038L$	$0.34 + 0.022L$	1.0	2
OR	4	$0.13 + 0.038L$	$0.45 + 0.025L$	1.0	3
NOT	1	$0.02 + 0.038L$	$0.05 + 0.017L$	1.0	1
NAND	2	$0.05 + 0.038L$	$0.08 + 0.027L$	1.0	1
NAND	3	$0.07 + 0.038L$	$0.09 + 0.039L$	1.0	2
NAND	4	$0.10 + 0.037L$	$0.12 + 0.051L$	1.0	2
NAND	5	$0.21 + 0.038L$	$0.34 + 0.019L$	1.0	4
NAND	6	$0.24 + 0.037L$	$0.36 + 0.019L$	1.0	5
NAND	8	$0.24 + 0.038L$	$0.42 + 0.019L$	1.0	6
NOR	2	$0.06 + 0.075L$	$0.07 + 0.016L$	1.0	1
NOR	3	$0.16 + 0.111L$	$0.08 + 0.017L$	1.0	2
NOR	4	$0.23 + 0.149$	$0.08 + 0.017L$	1.0	4
NOR	5	$0.38 + 0.038L$	$0.23 + 0.018L$	1.0	4
NOR	6	$0.46 + 0.037L$	$0.24 + 0.018L$	1.0	5
NOR	8	$0.54 + 0.038L$	$0.23 + 0.018L$	1.0	6
XOR	2*	$0.30 + 0.036L$	$0.30 + 0.021L$	1.1	3
		$0.16 + 0.036L$	$0.15 + 0.020L$	2.0	

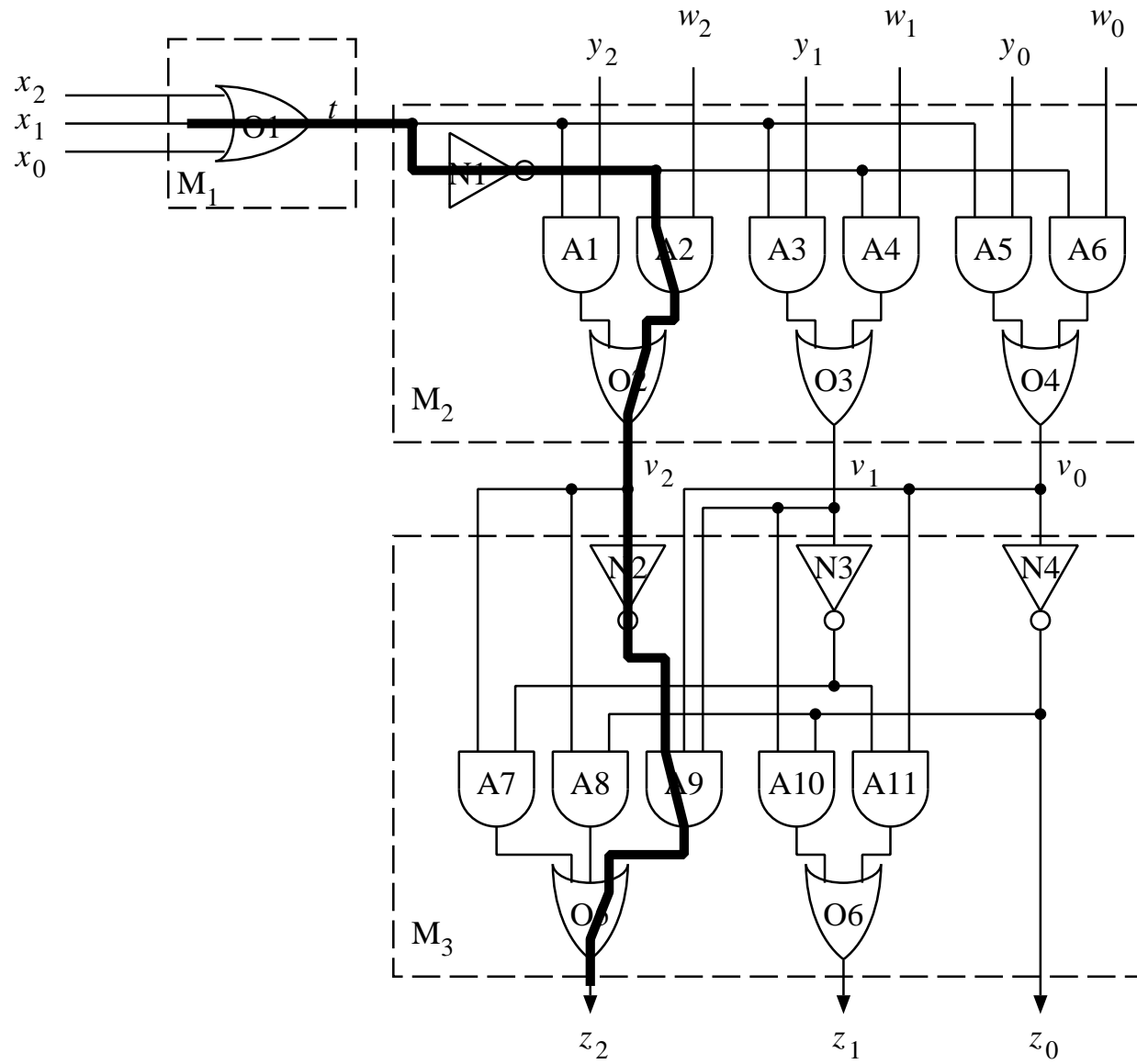


Figure 4.14: Network for hierarchical analysis

## Example (cont.)

---

Types of gates used: 2-input AND, 3-input AND, etc.

*Load factors.* network inputs: 1; gate inputs: 1

*Fanout factors.*  $F = 12$  (assumed)

$$F(z_2) = F(z_1) = 12, \quad F(z_0) = 12 - 2 = 10$$

*Network size :* 38 [equiv. gates] 21 [actual]

*Number of levels:* 7

*Network delay* The longest path:

$$O_1 \rightarrow N_1 \rightarrow A_2 \rightarrow O_2 \rightarrow N_2 \rightarrow A_9 \rightarrow O_5$$

$$T_{pLH}(x_1, z_2) = t_{pLH}(O_1) + t_{pHL}(N_1) + t_{pHL}(A_2) + t_{pHL}(O_2) \\ + t_{pLH}(N_2) + t_{pLH}(A_9) + t_{pLH}(O_5)$$

$$T_{pHL}(x_1, z_2) = t_{pHL}(O_1) + t_{pLH}(N_1) + t_{pLH}(A_2) + t_{pLH}(O_2) \\ + t_{pHL}(N_2) + t_{pHL}(A_9) + t_{pHL}(O_5)$$

Gate	Identifier	Output load	$t_{pLH}$ [ns]	$t_{pHL}$ [ns]
OR3	$O_1$	4	0.27	0.43
NOT	$N_1$	3	0.13	0.10
AND2	$A_2$	1	0.19	0.18
OR2	$O_2$	3	0.23	0.26
NOT	$N_2$	1	0.06	0.07
AND3	$A_9$	1	0.24	0.20
OR3	$O_5$	$L$	$0.12 + 0.038L$	$0.34 + 0.022L$

$$T_{pLH}(x_1, z_2) = 0.27 + 0.10 + 0.18 + 0.26 + 0.06 \\ + 0.24 + 0.12 + 0.038L = 1.23 + 0.038L \text{ [ns]}$$

$$T_{pHL}(x_1, z_2) = 0.43 + 0.13 + 0.19 + 0.23 + 0.07 \\ + 0.20 + 0.34 + 0.022L = 1.59 + 0.022L \text{ [ns]}$$

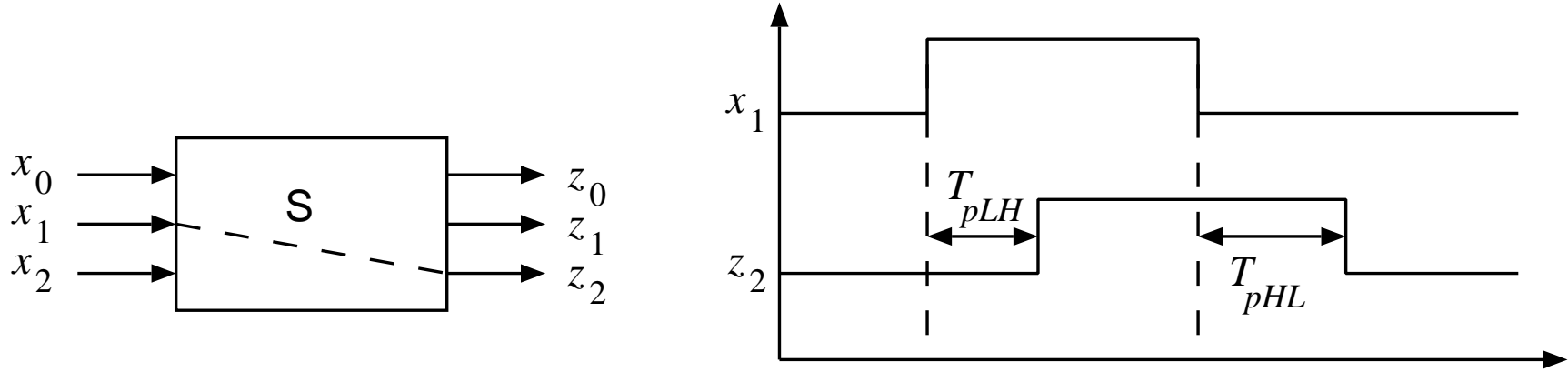


Figure 4.15: Timing diagram from network analysis