



Gate Networks

| | |
|--|---------------------------|
| 🔍 course | |
| ▼ area | ucla |
| 🕒 created | @January 17, 2023 2:15 PM |
| 🕒 updated | @January 17, 2023 3:49 PM |
| ↗️ <input checked="" type="checkbox"/> tasks | |
| ↗️ <input type="checkbox"/> courses | |
| 🔗 URL | |
| ▼ tags | CS |

Definitions



Big Ideas

▼ Combinational Module (Gate Networks)

- ▼ created with Gate Networks
- ▼ eg. set {AND,OR} gate network

Resources

<https://s3-us-west-2.amazonaws.com/secure.notion-static.com/4a2e7da1-0bfa-476f-b5fe-56eee9bf2fa1/ch4.pdf>

https://s3-us-west-2.amazonaws.com/secure.notion-static.com/338429c3-6e7f-4eed-9458-cd59d1a6bf4/cs51a_CriticalPath.pdf

 


Figure 4.2: A gate network

▼ logic diagram (graphical representation)

 


Figure 4.4: a) Graphical representation (logic diagram)

▼ net list (tabular representation)

| Gate | Type | Inputs | Output |
|------|---------|--|----------------|
| A | AND - 2 | A ₁ A ₂ | A ₃ |
| B | AND - 3 | B ₁ B ₂ B ₃ | B ₄ |
| C | OR - 2 | C ₁ C ₂ | C ₃ |

Gates

| From | To |
|----------------|----------------|
| x ₃ | A ₁ |
| x ₂ | A ₂ |
| x ₂ | B ₁ |
| x ₁ | B ₂ |
| x ₀ | B ₃ |
| A ₃ | C ₁ |
| B ₄ | C ₂ |
| C ₃ | z |

Connections

(b)

▼ Hardware Description Language (HDL) (program)

```

A_3 <= x3 and x2;
B_4 <= x2 and x1 and x0;
C_3 <= A_3 or B_4;
z    <= C_3;

```

(c)

▼ Universal Gates: {NAND, NOR}

▼ Universal Sets

▼ you can show a set of gates of a combinatorial module (gate network) is universal if it can be represented using only universal gates {NAND, NOR}

▼ e.g. NOT (inverter) and AND using universal gates


 


Figure 4.7: Implementations with NAND gates: a) NOT; b) AND

▼ Mixed-logic Notation and Complex gate structures

 ▼ e.g. showing gates as re-implemented unique gates



Complex gate structures

13


 


Figure 4.9: Additional gates in CMOS a) XOR and XNOR, b) Complex gate structures: AND-NOR and OR-NAND

▼ Critical Path: Dynamic Programming - Longest Path

▼ gates have delay time in execution → finding the largest latency in the gate network tells us how fast the network will execute (the slowest chain)

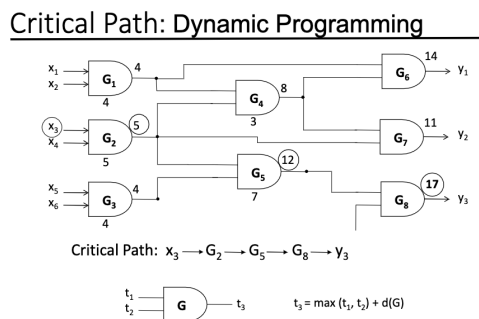
▼ the latency can be written above the gate



$$t_{\text{tot}} = t_n = \max(t_1, \dots, t_{n-1}) + d(G)$$

▼ Calculate Critical Path with Delay Table

 ▼ note how each gate changes its values as shown in the example



▼ the gate values are determined considering if inputs are all low (usually 0) then if inputs are all high (usually 1)

▼ e.g. gate A has low = 0 (bc with low inputs AND give 0) and has high = 1 (bc AND w high inputs gives 1) and o on

▼ use the delay table s.t. L = load factor = fan-out in the propagation delays

Table 4.3: Characteristics of a family of CMOS gates

| Gate type | Fan-in | Propagation delays | | Load factor [standard loads] | Size [equiv. gates] |
|-----------|--------|--------------------|-------------------|---------------------------------|------------------------|
| | | t_{pLH} [ns] | t_{pHL} [ns] | | |
| AND | 2 | $0.15 + 0.037L$ | $0.16 + 0.017L$ | 1.0 | 2 |
| AND | 3 | $0.20 + 0.038L$ | $0.18 + 0.018L$ | 1.0 | 2 |
| AND | 4 | $0.28 + 0.039L$ | $0.21 + 0.019L$ | 1.0 | 3 |
| OR | 2 | $0.12 + 0.037L$ | $0.20 + 0.019L$ | 1.0 | 2 |
| OR | 3 | $0.12 + 0.038L$ | $0.34 + 0.022L$ | 1.0 | 2 |
| OR | 4 | $0.13 + 0.038L$ | $0.45 + 0.025L$ | 1.0 | 3 |
| NOT | 1 | $0.02 + 0.038L$ | $0.05 + 0.017L$ | 1.0 | 1 |
| NAND | 2 | $0.05 + 0.038L$ | $0.08 + 0.027L$ | 1.0 | 1 |
| NAND | 3 | $0.07 + 0.038L$ | $0.09 + 0.039L$ | 1.0 | 2 |
| NAND | 4 | $0.10 + 0.037L$ | $0.12 + 0.051L$ | 1.0 | 2 |
| NAND | 5 | $0.21 + 0.038L$ | $0.34 + 0.019L$ | 1.0 | 4 |
| NAND | 6 | $0.24 + 0.037L$ | $0.36 + 0.019L$ | 1.0 | 5 |
| NAND | 8 | $0.24 + 0.038L$ | $0.42 + 0.019L$ | 1.0 | 6 |
| NOR | 2 | $0.06 + 0.075L$ | $0.07 + 0.016L$ | 1.0 | 1 |
| NOR | 3 | $0.16 + 0.111L$ | $0.08 + 0.017L$ | 1.0 | 2 |
| NOR | 4 | $0.23 + 0.149L$ | $0.08 + 0.017L$ | 1.0 | 4 |
| NOR | 5 | $0.38 + 0.038L$ | $0.23 + 0.018L$ | 1.0 | 4 |
| NOR | 6 | $0.46 + 0.037L$ | $0.24 + 0.018L$ | 1.0 | 5 |
| NOR | 8 | $0.54 + 0.038L$ | $0.23 + 0.018L$ | 1.0 | 6 |
| XOR | 2* | $0.30 + 0.036L$ | $0.30 + 0.021L$ | 1.1 | 3 |
| | | $0.16 + 0.036L$ | $0.15 + 0.020L$ | 2.0 | |

▼ delay prop. Low → High if gate has (0/1) and High → Low if (1/0) otherwise (0/0) and (1/1) have t=0 delay)

▼ fan-in in is the number of input variables

▼ fan-out is the number of output variables

- ▼ load factor is a reference to the energy/cost it takes to use the gate

- ▼ size is arbitrary definition based on power consumption and delay prop.

- ▼ size is now obsolete as transistors can be manufacture in billions to trillions per die

▼ Analysis of Gate Networks

▼ Functional Analysis

- ▼ define I/O switching expressions (typically letters with subscript)

- ▼ create a net list (tabular representation) of the binary function

- ▼ define high-level I/O variables
→ use codes to represent as bit-vectors

- ▼ create a high-level spec of the system

▼ Network characteristic

- ▼ input load factors

- ▼ fan-out factors

- ▼ delays

- ▼ e.g. logic diagram with SEs

 


Figure 4.10: Gate network for analysis

▼ e.g. binary function

Output expressions:

$$\begin{aligned}
 z_0 &= T_2 + T_3 \\
 &= x_0'x_1'x_2 + x_0T_1 \\
 &= x_0'x_1'x_2 + x_0(x_2' + x_3) \\
 &= x_0'x_1'x_2 + x_0x_2' + x_0x_3 \\
 \\
 z_1 &= T_5 + T_6 \\
 &= x_1x_2x_3 + T_4' \\
 &= x_1x_2x_3 + (T_1x_0'x_1)' \\
 &= x_1x_2x_3 + T_1' + x_0 + x_1' \\
 &= x_1x_2x_3 + x_2x_3' + x_0 + x_1'
 \end{aligned}$$

Reduced expressions

$$\begin{aligned}
 z_0 &= x_0'x_1'x_2 + x_0x_2' + x_0x_3 \quad (\text{no reduction possible}) \\
 z_1 &= x_0 + x_1' + x_2
 \end{aligned}$$

▼ Hierarchical approach

- ▼ decompose the network in subnetworks (modules)
- ▼ analyze subnetworks separately
- ▼ substitute into gate network function
- ▼ e.g. creating subnetworks

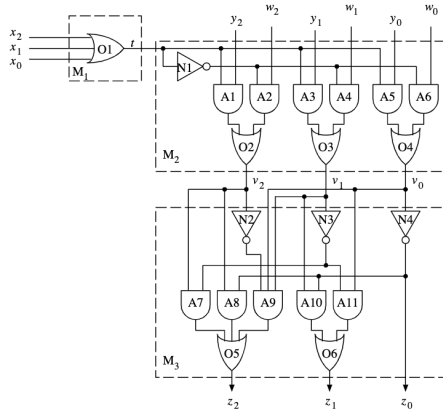


Figure 4.11: Network for hierarchical analysis

▼ verify subnetwork satisfies binary function

▼ binary function (spec)

Inputs: $x, y, w \in \{0, 1, \dots, 7\}$

Output: $z \in \{0, 1, \dots, 7\}$

Function: $z = \begin{cases} (y + 1) \bmod 8 & \text{if } x \neq 0 \\ (w + 1) \bmod 8 & \text{if } x = 0 \end{cases}$

▼ subnetwork functions

M_1 :

$$t = x_2 + x_1 + x_0$$

$$t = \begin{cases} 1 & \text{if } x \neq 0 \\ 0 & \text{otherwise} \end{cases}$$

M_2 :

$$v_i = y_i t + w_i t' \quad (i = 0, 1, 2)$$

$$v = \begin{cases} y & \text{if } t = 1 \\ w & \text{if } t = 0 \end{cases}$$

$$v = \begin{cases} y & \text{if } t = 1 \\ w & \text{if } t = 0 \end{cases}$$

M_3 :

$$z_2 = v'_2 v_1 v_0 + v_2 v'_1 + v_2 v'_0$$

$$z_1 = v_1 v'_0 + v'_1 v_0$$

$$z_0 = v'_0$$

▼ create high level spec (net list, table)

High-level specification:

| v_2 | v_1 | v_0 | z_2 | z_1 | z_0 | | v | z |
|-------|-------|-------|-------|-------|-------|---|-----|-----|
| 0 | 0 | 0 | 0 | 0 | 1 | | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 | | 1 | 2 |
| 0 | 1 | 0 | 0 | 1 | 1 | | 2 | 3 |
| 0 | 1 | 1 | 1 | 0 | 0 | → | 3 | 4 |
| 1 | 0 | 0 | 1 | 0 | 1 | | 4 | 5 |
| 1 | 0 | 1 | 1 | 1 | 0 | | 5 | 6 |
| 1 | 1 | 0 | 1 | 1 | 1 | | 6 | 7 |
| 1 | 1 | 1 | 0 | 0 | 0 | | 7 | 0 |

▼ derive network function

From table, we get

$$z = (v + 1) \bmod 8$$



SUMMARY