

- Design of two-level networks:
AND-OR and OR-AND networks
- Minimal two-level networks
Karnaugh maps
Minimization procedure and tools
Limitations of two-level networks
- Design of two-level NAND-NAND and NOR-NOR networks
- Programmable logic: PLAs and PALs.

Implementation:

Level 1 (optional) NOT gates

Level 2 AND gates

Level 3 OR gates

Literals

(uncomplemented and complemented variables)

NOT gates (if needed)

Products: AND gates

Sum: OR gate

Multioutput networks: one OR gate is used for each output

Product of sums networks - similar

Modulo-64 incrementer

Input: $0 \leq x \leq 63$

Output: $0 \leq z \leq 63$

Function: $z = (x + 1) \bmod 64$

$$\begin{array}{c|c} x & 010101 \\ \hline z & 010110 \end{array} \quad \begin{array}{c|c} x & 001111 \\ \hline z & 010000 \end{array}$$

- Radix-2 representation

$$z_i = \begin{cases} 1 & \text{if } (x_i = 1 \text{ and there exists } j < i \text{ such that } x_j = 0) \\ & \text{or } (x_i = 0 \text{ and } x_j = 1 \text{ for all } j < i) \\ 0 & \text{otherwise} \end{cases}$$

$$\begin{aligned} z_5 &= x_5(x'_4 + x'_3 + x'_2 + x'_1 + x'_0) + x'_5x_4x_3x_2x_1x_0 \\ &= x_5x'_4 + x_5x'_3 + x_5x'_2 + x_5x'_1 + x_5x'_0 + x'_5x_4x_3x_2x_1x_0 \\ z_4 &= x_4x'_3 + x_4x'_2 + x_4x'_1 + x_4x'_0 + x'_4x_3x_2x_1x_0 \\ z_3 &= x_3x'_2 + x_3x'_1 + x_3x'_0 + x'_3x_2x_1x_0 \\ z_2 &= x_2x'_1 + x_2x'_0 + x'_2x_1x_0 \\ z_1 &= x_1x'_0 + x'_1x_0 \\ z_0 &= x'_0 \end{aligned}$$

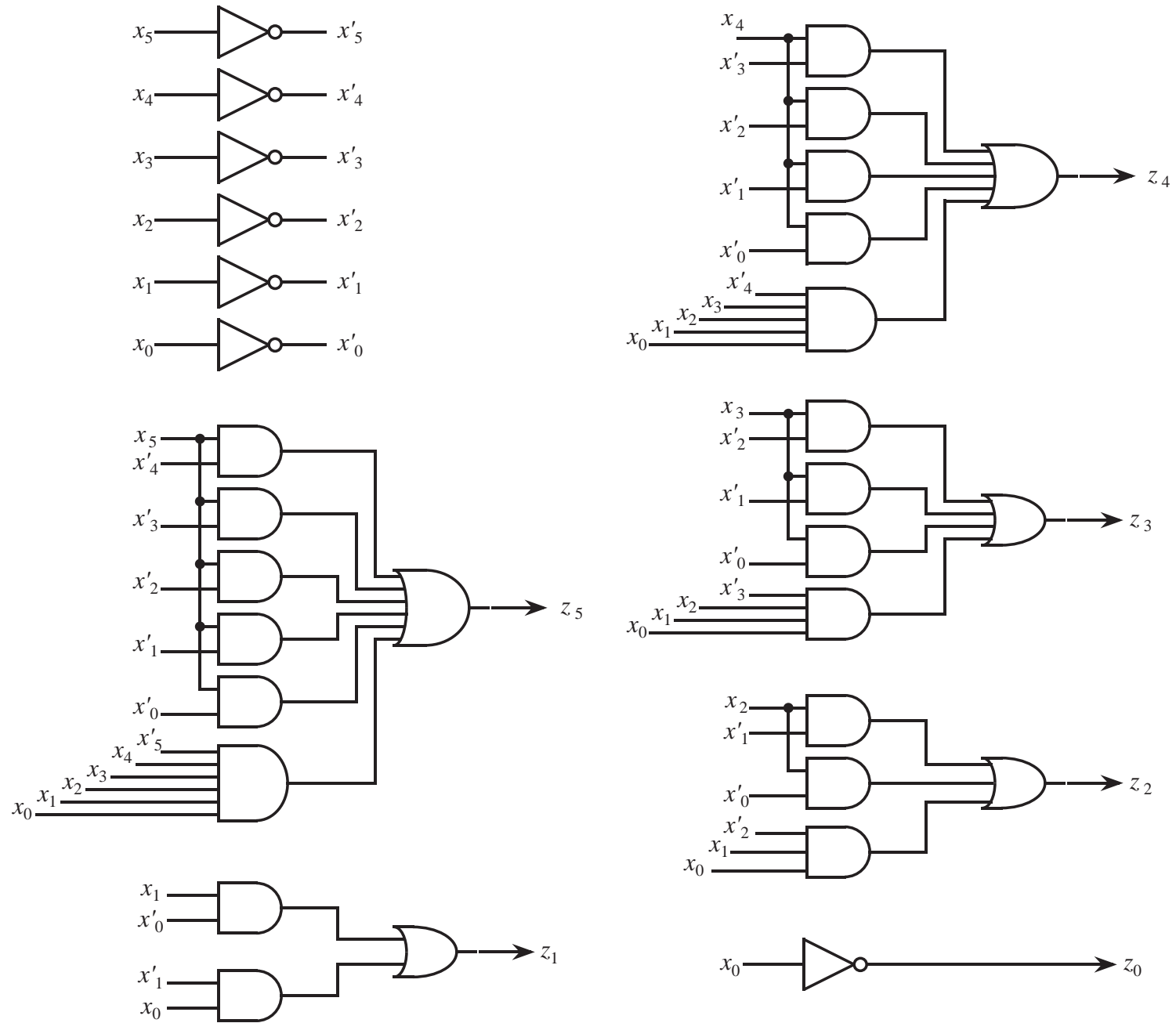


Figure 5.1: NOT-AND-OR modulo-64 incrementer network.

- Two types of two-level networks:

AND-OR **network** \Leftrightarrow Sum of products (NAND-NAND network)

OR-AND **network** \Leftrightarrow Product of sums (NOR-NOR network)


 


Figure 5.2: AND-OR and OR-AND networks.


$$E(x_2, x_1, x_0) = x_2'x_1'x_0 + x_2x_1 + x_1x_0'$$

$$E(x_2, x_1, x_0) = (x_2' + x_1)(x_1 + x_0')(x_2 + x_1' + x_0)$$

 1. Inputs: uncomplemented and complemented
2. Fanin unlimited
3. Single-output networks
4. Minimal network:
minimum number of gates with minimum number of inputs
(minimal expression: min. number of terms with min. number of literals)



Network A

 

Network B

Figure 5.3: Networks with different cost to implement $f(x_2, x_1, x_0) = \text{one-set}(3, 6, 7)$.

- Equivalent but different cost

$$E_1(x_2, x_1, x_0) = x_2'x_1x_0' + x_1'x_0 + x_2x_0$$

$$E_2(x_2, x_1, x_0) = x_2x_1x_0 + x_2'x_1x_0' + x_2'x_1'x_0 + x_2x_1'x_0$$

- Both minimal SP and PS must be obtained and compared
- Basis:

$$ab + ab' = a \quad (\text{for sum of products})$$



$$(a + b)(a + b') = a \quad (\text{for product of sums})$$

- 2-dimensional array of cells
- n variables $\longrightarrow 2^n$ cells
- cell $i \longleftrightarrow$ assignment i

adjacency condition

any set of 2^r adjacent rows (columns):
assignments differ in r variables

  
- representing switching functions
- representing switching expressions
- graphical aid in simplifying expressions




(a)

(b)

(c)

 

(d)

 

 


Figure 5.5: K-map for five variables

$$x_2 \left| \begin{array}{|c|c|c|c|} \hline & \overbrace{x_0} & & \\ \hline 1 & 0 & 0 & 1 \\ \hline 0 & 0 & 0 & 1 \\ \hline & \underbrace{x_1} & & \\ \hline \end{array} \right.$$

$$\begin{array}{c} \overline{x_0} \\ \begin{array}{|c|c|c|c|} \hline 1 & 0 & 0 & 1 \\ \hline 0 & 1 & 1 & 0 \\ \hline 1 & 0 & 1 & 1 \\ \hline 1 & 1 & 0 & 0 \\ \hline \end{array} \left. \vphantom{\begin{array}{|c|c|c|c|} \hline 1 & 0 & 0 & 1 \\ \hline 0 & 1 & 1 & 0 \\ \hline 1 & 0 & 1 & 1 \\ \hline 1 & 1 & 0 & 0 \\ \hline \end{array}} \right\} x_2 \\ \overline{x_1} \end{array}$$

$$x_2 \left| \begin{array}{cc|cc} & \overbrace{x_0} & & \\ \hline 1 & 0 & - & - \\ \hline 1 & 1 & 0 & 0 \\ \hline & \underbrace{x_1} & & \end{array} \right.$$

Rectangles of 1-cells and sum of products

1. Minterm m_j corresponds to 1-cell with label j .
2. Product term of $n - 1$ literals \longleftrightarrow rectangle of two adjacent 1-cells.

$$\begin{aligned}
 x_3 x_1' x_0 &= x_3 x_1' x_0 (x_2 + x_2') \\
 &= x_3 x_2 x_1' x_0 + x_3 x_2' x_1' x_0 \\
 &= m_{13} + m_9
 \end{aligned}$$

 


Figure 5.6

Rectangles of 1-cells and sum of products (cont.)

3. Product term of $n - 2$ literals \longleftrightarrow rectangle of four adjacent 1-cells.

$$\begin{aligned}
 x_3x_0 &= x_3x_0(x_1 + x'_1)(x_2 + x'_2) \\
 &= x_3x'_2x'_1x_0 + x_3x'_2x_1x_0 + x_3x_2x'_1x_0 + x_3x_2x_1x_0 \\
 &= m_9 + m_{11} + m_{13} + m_{15}
 \end{aligned}$$

 


Figure 5.6

4. Product term of $n - s$ literals \longleftrightarrow rectangle of 2^s adjacent 1-cells.

 
 
Figure 5.7: Representation of product of $n - (a + b)$ variables.

Figure 5.8: Product terms and rectangles of 1-cells.

Sum of products

represented in a K-map by the union of rectangles

$$E(x_3, x_2, x_1, x_0) = x'_3 x_2 x_1 + x'_2 x_1 x_0 + x'_0$$

				x_0			
				1	0	1	1
				1	0	1	1
				1	0	0	1
				1	0	1	1
x_3							
				x_1			
				x_2			

$$E(a, b, c) = ab + ac + b'c'$$

					c				
					1	0	0	0	0
					1	1	1	1	1
a									
					b				

Rectangles of 0-cells and product of sums

0-cell 13 corresponds to the maxterm

$$M_{13} = x'_3 + x'_2 + x_1 + x'_0$$

Rectangle of $2^a \times 2^b$ 0-cells \longleftrightarrow sum term of $n - (a + b)$ literals

Implicant: product term for which $f=1$

 


Figure 5.9: Implicant representation.

Implicants: $x'_3x'_2x'_1x_0$, all product terms with x_3 .

Prime Implicant: Implicant not covered by another implicant.

Prime implicants: $x'_2x'_1x_0$, x_3

Find all Pls

a) $f(x_2, x_1, x_0) = \text{one-set}(2, 4, 6)$

	x_0			
	0	0	0	1
x_2	1	0	0	1
	x_1			

Pls: $x_2x'_0$ and $x_1x'_0$

b) $f(x_2, x_1, x_0) = \text{one-set}(0, 1, 5, 7)$

	x_0			
	1	1	0	0
x_2	0	1	1	0
	x_1			

Pls: $x'_2x'_1$, x_2x_0 , and x'_1x_0

c) $f(x_3, x_2, x_1, x_0) = \text{one-set}(0, 3, 5, 7, 11, 12, 13, 15)$

x_0					
x_3	1	0	1	0	x_2
	0	1	1	0	
	1	1	1	0	
	0	0	1	0	
x_1					

Pls: x_2x_0 , x_1x_0 , $x_3x_2x'_1$, and $x'_3x'_2x'_1x'_0$

Minimal sum of products consists of prime implicants

 


Figure 5.10: Minimal sum of products and prime implicants.

Example 5.9

$$E(x_2, x_1, x_0) = x_2x_1'x_0' + x_2x_1x_0' + x_1x_0'$$

				x_0		
$x_2x_1'x_0'$		0	0	0	1	x_1x_0'
x_2	1	0	0	0	1	$x_2x_1x_0'$
x_2x_0'				x_1		

not PIs: $x_2x_1'x_0'$ and $x_2x_1x_0'$

PI: x_2x_0' , x_1x_0'

reduced SP: $E(x_2, x_1, x_0) = x_2x_0' + x_1x_0'$

Essential Prime Implicants (EPI)

$p_e(\underline{a}) = 1$ and $p(\underline{a}) = 0$ for any other PI p

	x_0			
x_2	1		1	
	1		1	1
	x_1			

EPIs: $x_1'x_0'$ and x_1x_0

non-essential: x_2x_1 , x_2x_0' .

- All EPIs are included in a minimal SP

Procedure for finding min SP

1. Determine all PIs
2. Obtain the EPIs
3. If not all 1-cells covered, choose a cover from the remaining PIs

Example 5.10

Find a minimal SP:

a) $E(x_3, x_2, x_1, x_0) = x'_3x'_2 + x'_3x_2x_0 + x_1x_0$

x_0			
1	1	1	1
	1	1	
		1	
		1	
x_1			
x_3		x_2	

- Pls: $x'_3x'_2$, x'_3x_0 , and x_1x_0
- all EPIs
- unique min SP: $x'_3x'_2 + x'_3x_0 + x_1x_0$

b) $E(x_2, x_1, x_0) = \Sigma m(0, 3, 4, 6, 7)$

	x_0	
	1	1
x_2	1	1
	x_1	

- Pls: $x_1'x_0'$, x_1x_0 , x_2x_0' , and x_2x_1
- EPIs: $x_1'x_0'$ and x_1x_0
- extra cover: x_2x_0' or x_2x_1
- Two min SPs:

$$x_1'x_0' + x_1x_0 + x_2x_0' \quad \text{and} \quad x_1'x_0' + x_1x_0 + x_2x_1$$

c) $E(x_2, x_1, x_0) = \Sigma m(0, 1, 2, 5, 6, 7)$

	x_0			
	1	1		1
x_2		1	1	1
	x_1			

- Pls: $x'_2x'_1$, $x'_2x'_0$, x_2x_0 , x_2x_1 , x'_1x_0 , and $x_1x'_0$
- No EPIs
- Two min SPs

$$x'_2x'_1 + x_2x_0 + x_1x'_0 \quad \text{and} \quad x'_2x'_0 + x'_1x_0 + x_2x_1$$

Minimal SPs for incompletely specified functions

		x_0				
		1	0	1	0	
		0	-	1	0	
	x_3	1	-	0	-	x_2
		1	0	-	-	
		x_1				

A minimal SP

$$E(x_3, x_2, x_1, x_0) = x_3x'_0 + x'_3x_0 + x'_3x'_2x'_1$$

Minimization of products of sums

Implicate: sum term for which $f = 0$.

Prime Implicate: implicate not covered by another implicate

Essential prime implicate: at least one "cell" not included in other implicate

$$f(x_3, x_2, x_1, x_0) = \text{zero-set}(7, 13, 15)$$

x_0				x_2			
1	1	1	1				
1	1	0	1				
1	0	0	1				
x_1				x_3			
1	1	1	1				
1	1	1	1				
1	1	1	1				

The prime implicates: $(x'_3 + x'_2 + x'_0)$ and $(x'_2 + x'_1 + x'_0)$

Both essential.

Procedure for finding min PS

1. Determine all prime implicants
2. Determine the essential prime implicants
3. From set of nonessential prime implicants, select cover of remaining 0-cells

		x_0			
		1	1	1	0
		1	0	0	1
		1	0	0	1
		1	1	1	0
		x_1			
x_3					x_2

- The prime implicants: $(x'_0 + x'_2)$ and $(x_0 + x_2 + x'_1)$
- Both essential, the minimal PS is $(x'_0 + x'_2)(x_0 + x_2 + x'_1)$

Function: $z = \begin{cases} 1 & \text{if } x \in \{0, 2, 3, 5, 8\} \\ 0 & \text{otherwise} \end{cases}$

The values $\{10,11,12,13,14,15\}$ are “don’t cares”

$$\min \text{ PS: } z = (x'_2 + x'_1)(x'_2 + x_0)(x_2 + x_1 + x'_0)$$

 


Figure 5.11: Minimal AND-OR network

Example 5.15

Input: $x \in \{0, 1, 2, \dots, 15\}$
 represented in binary code by $\underline{x} = (x_3, x_2, x_1, x_0)$
 Output: $z \in \{0, 1\}$

Function: $z = \begin{cases} 1 & \text{if } x \in \{0, 1, 3, 5, 7, 11, 12, 13, 14\} \\ 0 & \text{otherwise} \end{cases}$

The K-map:

			x_0	
			+	
			1	0
			1	0
			1	0
			0	1
			0	0
			1	0
			0	0
			+	
			+	
			x_1	

$$\text{min SP: } z = x'_3x_0 + x'_3x'_2x'_1 + x_2x'_1x_0 + x_3x_2x'_0 + x'_2x_1x_0$$

$$\text{min PS: } z = (x'_3 + x_2 + x_1)(x_3 + x'_2 + x_0)(x_2 + x'_1 + x_0)(x'_3 + x'_2 + x'_1 + x'_0)$$

$$\text{Cost(PS)} < \text{Cost(SP)}$$

 


Figure 5.12: Minimal OR-AND network

Design of multiple-output two-level gate networks

- Separate network for each output: no sharing

Example 5.16

Inputs: $(x_2, x_1, x_0), \quad x_i \in \{0, 1\}$

Output: $z \in \{0, 1, 2, 3\}$

Function: $z = \sum_{i=0}^2 x_i$

1. The switching functions in tabular form are

x_2	x_1	x_0	z_1	z_0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

2. The corresponding K-maps are

$$\begin{array}{c}
 z_1 \\
 \begin{array}{c} x_0 \\ \hline
 \begin{array}{|c|c|c|c|}
 \hline
 0 & 0 & 1 & 0 \\
 \hline
 0 & 1 & 1 & 1 \\
 \hline
 \end{array} \\
 x_2 \\
 \hline
 x_1
 \end{array}
 \end{array}$$

$$\begin{array}{c}
 z_0 \\
 \begin{array}{c} x_0 \\ \hline
 \begin{array}{|c|c|c|c|}
 \hline
 0 & 1 & 0 & 1 \\
 \hline
 1 & 0 & 1 & 0 \\
 \hline
 \end{array} \\
 x_2 \\
 \hline
 x_1
 \end{array}
 \end{array}$$

3. minimal SPs:

$$z_1 = x_2x_1 + x_2x_0 + x_1x_0$$

$$z_0 = x_2'x_1'x_0 + x_2'x_1x_0' + x_2x_1'x_0' + x_2x_1x_0$$

4. minimal PSs:

$$z_1 = (x_2 + x_0)(x_2 + x_1)(x_1 + x_0)$$

$$\begin{aligned}
 z_0 = & (x_2 + x_1 + x_0)(x_2 + x_1' + x_0') \\
 & (x_2' + x_1 + x_0')(x_2' + x_1' + x_0)
 \end{aligned}$$

5. SP and PS expressions have the same cost

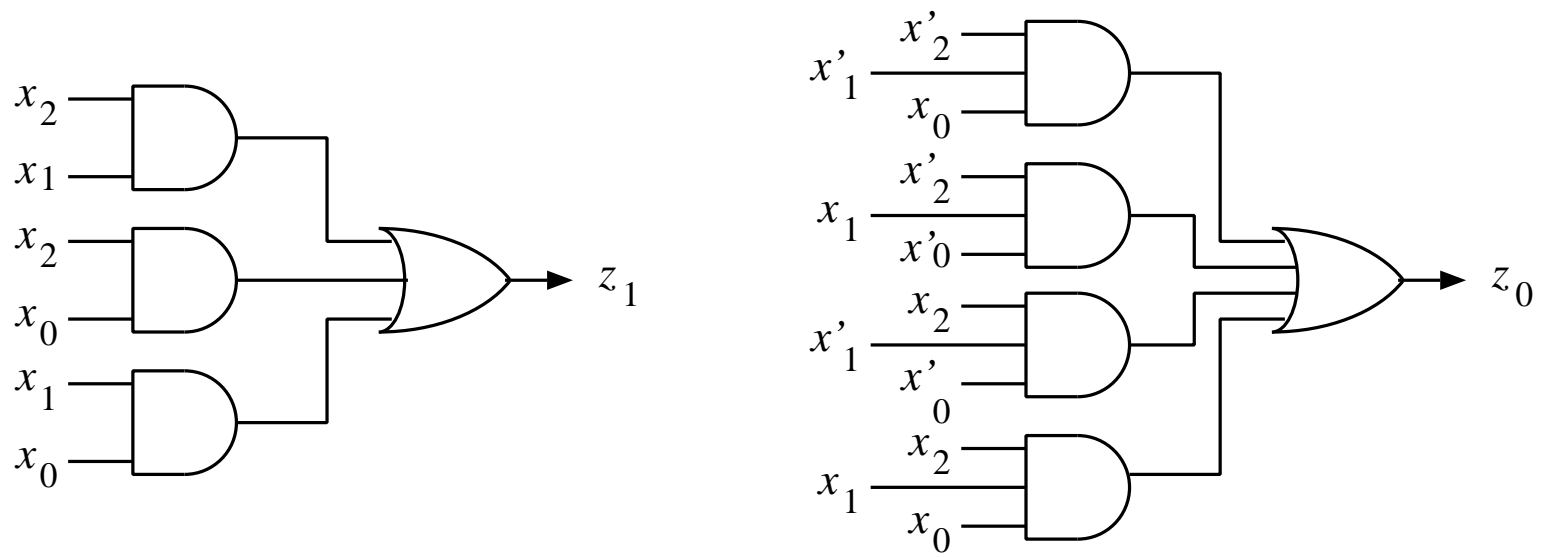


Figure 5.13: Minimal two-output AND-OR network

Two-level NAND-NAND and NOR-NOR networks

$$E = p_1 + p_2 + p_3 + \dots + p_n$$

p_1, p_2, \dots are product terms

$$E = (p'_1 \cdot p'_2 \cdot p'_3 \dots p'_n)'$$

or

$$E = \text{NAND}(\text{NAND}_1, \text{NAND}_2, \text{NAND}_3, \dots, \text{NAND}_n)$$

 


Figure 5.15: Transformation of AND-OR network into NAND network

Example: NOR network

$$z = x'_5(x_4 + x'_3)(x_2 + x_1 + x_0)$$

 


Figure 5.16: Equivalent OR-AND and NOR networks


Limitations of two-level networks

1. The requirement of uncomplemented and complemented inputs
If not satisfied, an additional level of NOT gates needed
2. A two-level implementation of a function might require a large number of gates and irregular connections
3. Existing technologies have limitations in the fan-in of the gates
4. The procedure essentially limited to the single-output case
5. The cost criterion of minimizing the number of gates is not adequate for many MSI/LSI/VLSI designs

Programmable Modules: PLAs and PALs

- Standard (fixed) structure
- Customized (programmed) for a particular function
 - during the last stage of fabrication
 - when incorporated into a system
- Flexible use
- More expensive and slower than fixed-function modules
- Other types discussed in Chapter 12

Figure 5.17: Programmable logic array (PLA): a) block diagram; b) logic diagram.

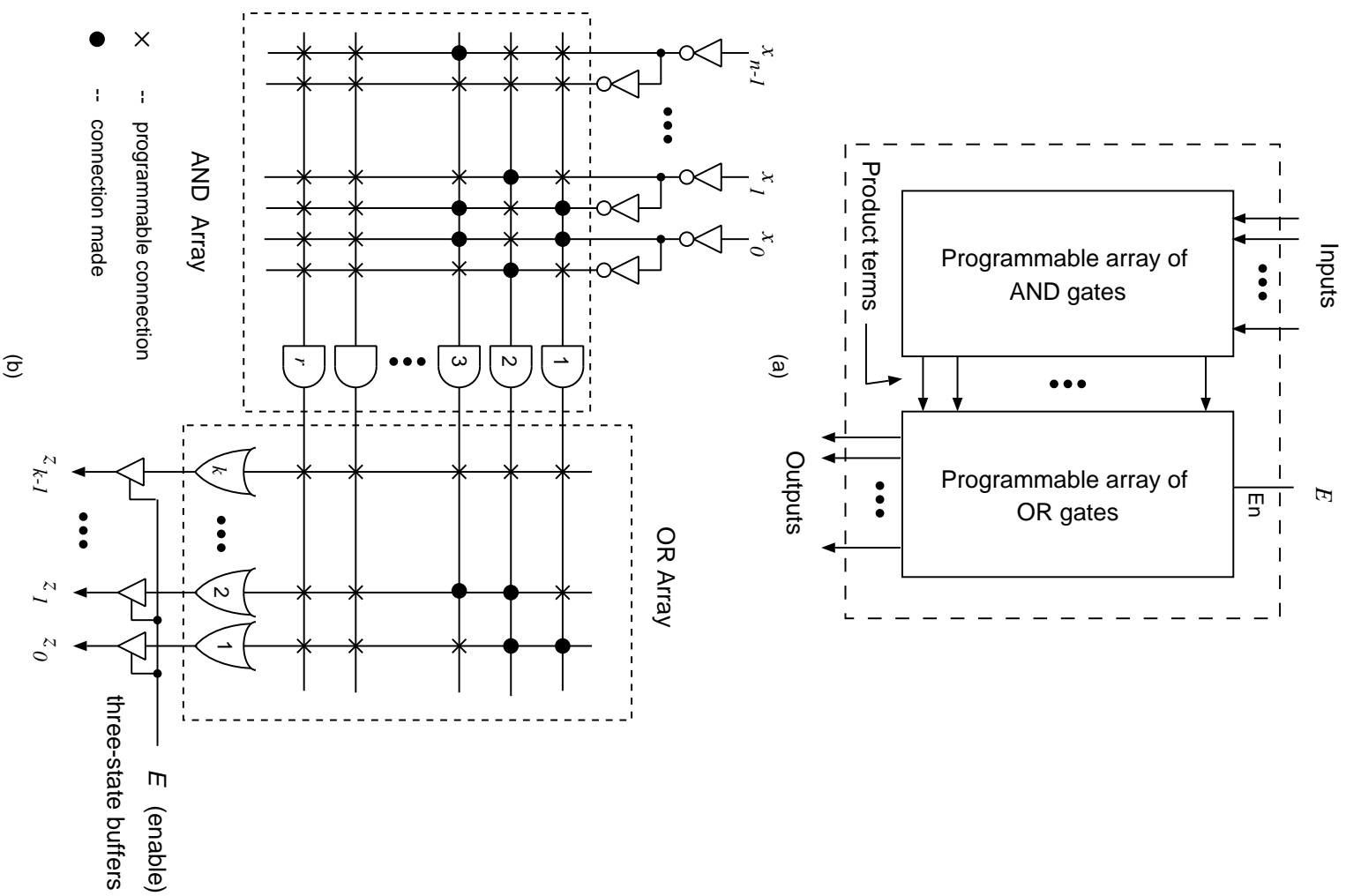

MOS PLA (OR-AND version)

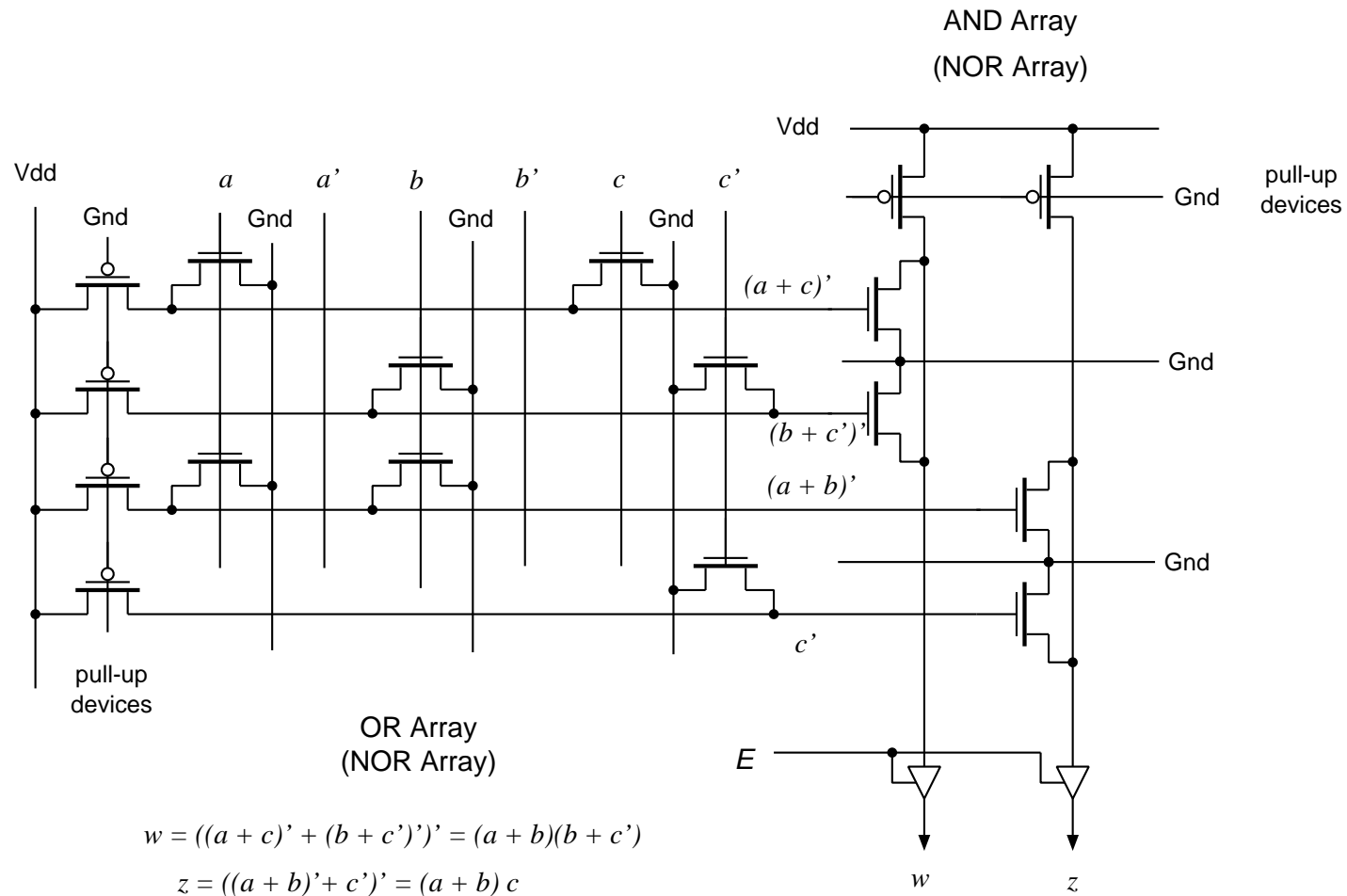


Figure 5.18: Example of PLA implementation at the circuit level: fragment of a MOS PLA.

Implementation of switching functions using PLAs

A BCD-to-Gray converter

Inputs: $\underline{d} = (d_3, d_2, d_1, d_0)$, $d_j \in \{0, 1\}$

Outputs: $\underline{g} = (g_3, g_2, g_1, g_0)$, $g_j \in \{0, 1\}$

Function:

i	$d_3d_2d_1d_0$	$g_3g_2g_1g_0$
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100
9	1001	1101

Expressions:

$$g_3 = d_3$$

$$g_2 = d_3 \oplus d_2$$

$$g_1 = d_2' d_1 \oplus d_2 d_1'$$

$$g_0 = d_1 d_0' \oplus d_1' d_0$$

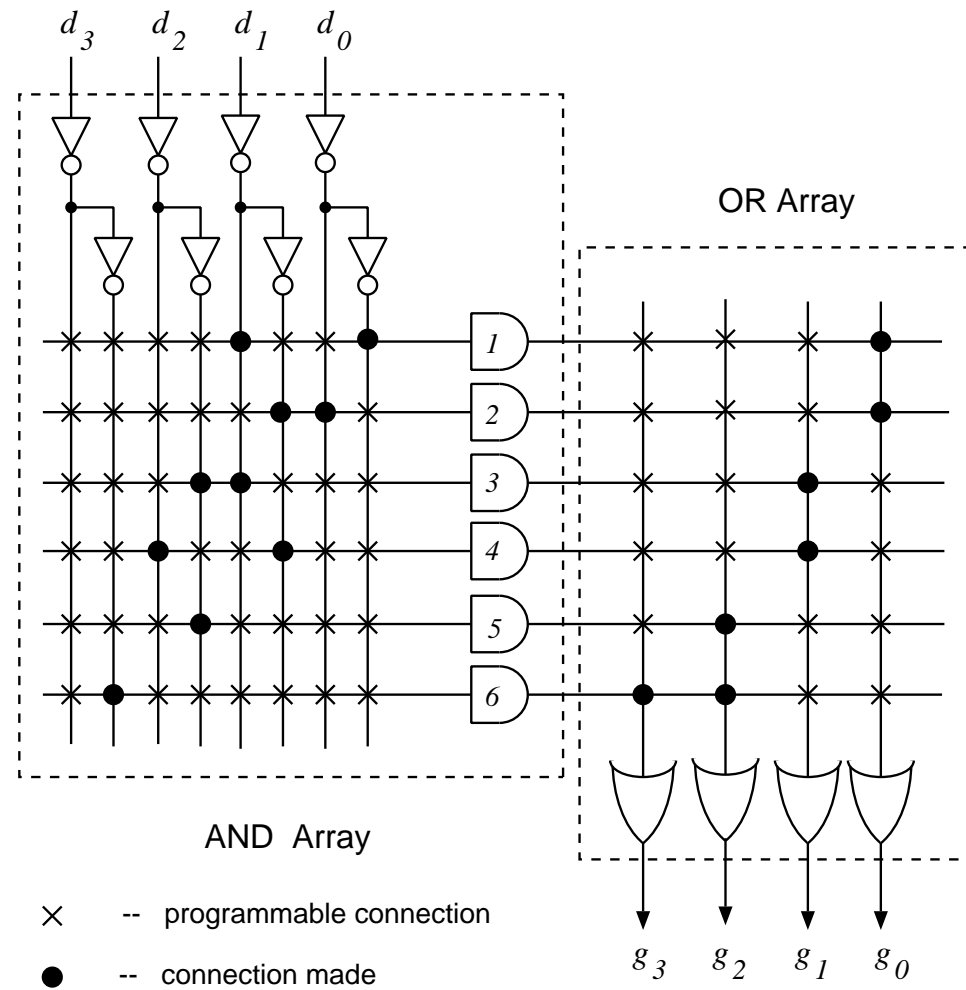


Figure 5.19: PLA implementation of BCD-Gray code converter.

PAL : a programmable module with fixed OR array

- Faster, more inputs and product terms compared to PLAs

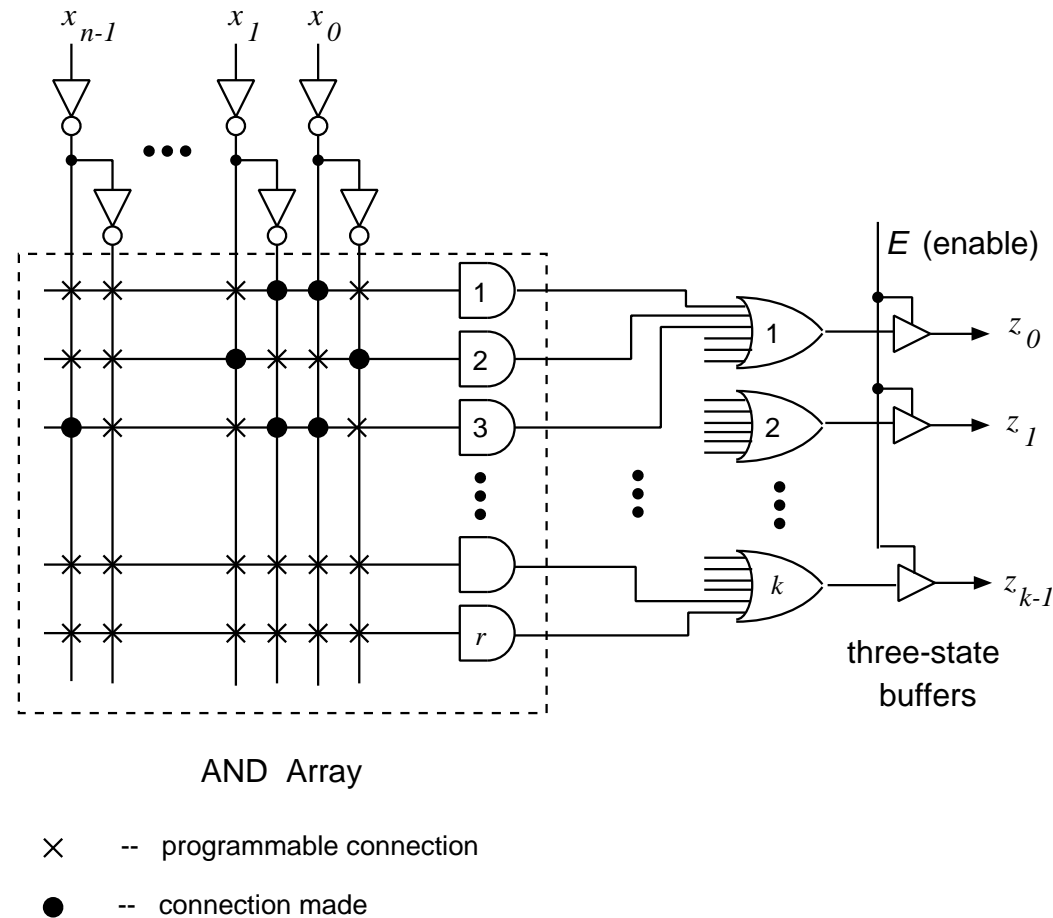


Figure 5.20: Logic diagram of a PAL

Figure 5.21: 16-input, 8-output PAL(P16H8)

